 


Computer Architecture Homework 4

Spring 2023, March

1 Boolean Algebra and Logic Gates

For the circuit shown below:



- a. Write the Boolean Expression of the circuit and simplify it step by step (as simple as possible). (10 pts)

$$\text{output} = \bar{A}\bar{B} + C(\bar{C} + BC + \bar{A}\bar{A})$$

$$= \bar{A}\bar{B} + C\bar{C} + BCC + \bar{A}\bar{A}C$$

$$= \bar{A}\bar{B} + BC + \bar{A}C$$

$$= \bar{A}\bar{B} + BC + \bar{A}C C B + \bar{B})$$

$$= \bar{A}\bar{B} + BC + \bar{A}BC + \bar{A}\bar{B}C$$

$$= \bar{A}\bar{B}C(1+C) + BC(1+\bar{A})$$

$$= \bar{A}\bar{B} + BC$$

唯一一个有变化的
(B, \bar{B})

b. Write the Truth Table of the simplified Boolean Expression. (10 pts)


A	B	C	Output
1	1	1	1
1	1	0	0
1	0	1	0
1	0	0	0
0	1	1	1
0	1	0	0
0	0	1	1
0	0	0	1

c. Create a circuit of Boolean Expression $Y = A + B$ using only NAND gates. (10 pts)

$$\overline{AB} = \overline{A} + \overline{B}$$


$$\overline{A} = \overline{AA}$$
 
$$Y = A + B = \overline{\overline{A} + \overline{B}} = \overline{\overline{A} \overline{B}} = \overline{\overline{AA} \overline{BB}}$$




2 FSM

a.

 

- (1) (5 pts) Start with the initial state, the FSM outputs a 1 if it detects the pattern (bitstring) : two or more successive '1'
- (2) (5 pts) What would it output for the input bitstring "011001110"?
001000110

 b. Draw a FSM that outputs 1 when it receives two or more successive '0'. Complete the following graph. (20 pts)




c. Fill out the remainder of the table for the FSM in (b). (10 pts)

Input	-	1	0	0	1	0	1	0	0
Next State	A	<u>A</u>	<u>B</u>	<u>C</u>	<u>A</u>	<u>B</u>	<u>A</u>	<u>B</u>	<u>C</u>
Output	-	<u>0</u>	<u>0</u>	<u>1</u>	<u>0</u>	<u>0</u>	<u>0</u>	<u>0</u>	<u>1</u>

3 SDS

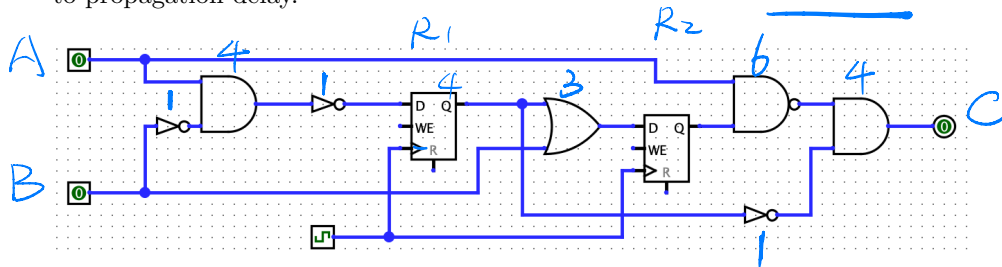In the following circuit, NOT gates have a delay of 1ns, AND gates have a delay of 4ns, NAND gates have a delay of 6ns, OR gates have a delay of 3ns. The registers have a clk-to-q delay of 4ns and setup times of 6ns. Assume the inputs comes from registers and output is connected to a register. All the delays refer to propagation delay.



- a. What is the minimum acceptable clock cycle time for this circuit? What clock frequency does it correspond to? (please include enough explanation) (20 pts)

$$T_{clk} \geq t_{pcq} + t_{pd} + \text{set up}$$

$$R_1: B \rightarrow \text{NOT} \rightarrow \text{AND} \rightarrow \text{NOT} \rightarrow R_1 \quad T_{clk} \geq 4 + 1 + 4 + 1 + 6 = 16 \text{ ns}$$

$$R_2: B \rightarrow \text{OR} \rightarrow R_2$$

$$T_{clk} \geq 4 + 3 + 6 = 13 \text{ ns}$$

$$C: R_2 \rightarrow \text{NAND} \rightarrow \text{AND} \rightarrow C$$

$$T_{clk} \geq 4 + 6 + 4 + 6 = 20 \text{ ns}$$

$$\therefore T_{clk} \geq 20 \text{ ns}$$

$$\text{or } T_{clk} = 20 \text{ ns}$$

$$\therefore f = \frac{1}{T_{clk}} = \frac{1}{20 \times 10^{-9}} = 50 \text{ MHz}$$

- b. What is the maximum allowable hold time for the registers that allows this circuit run correctly? (please include enough explanation) (10 pts)

$$t_{cd} \geq \text{hold time} - t_{ccq} \Rightarrow \text{hold time} \leq t_{cd} + t_{ccq}$$

$$R_1: R_1 \rightarrow \text{OR} \rightarrow R_2 \quad \text{hold time} \leq 3 + 4 = 7 \text{ ns}$$

$$R_2: R_2 \rightarrow \text{NAND} \rightarrow \text{AND} \rightarrow C \quad \text{hold time} \leq 6 + 4 + 4 = 14 \text{ ns}$$

$$A: A \rightarrow \text{AND} \rightarrow \text{NOT} \rightarrow R_1 \quad \text{hold time} \leq 4 + 1 + 4 \leq 9 \text{ ns}$$

$$B: B \rightarrow \text{OR} \rightarrow R_2 \quad \text{hold time} \leq 3 + 4 \leq 7 \text{ ns}$$

$$\therefore \text{hold time} \leq 7 \text{ ns}$$

$$\therefore (\text{hold time})_{\max} = 7 \text{ ns}$$